

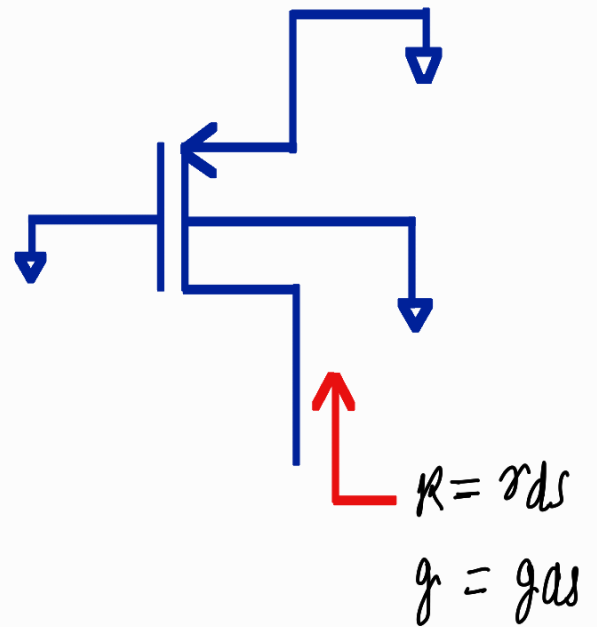
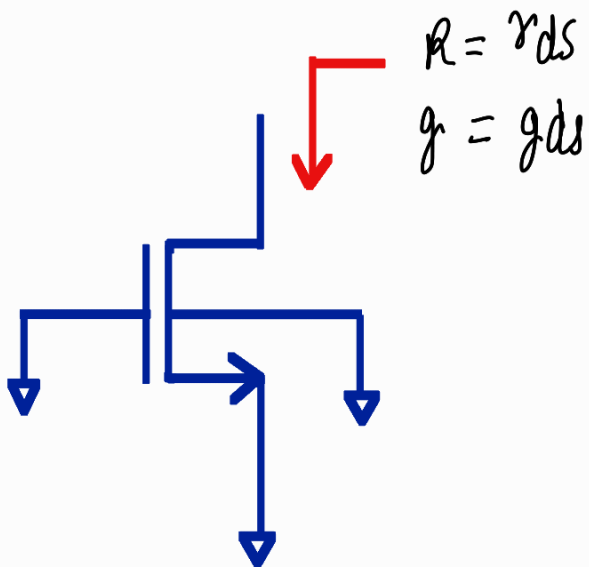


Looking into the Node

① Looking into Drain

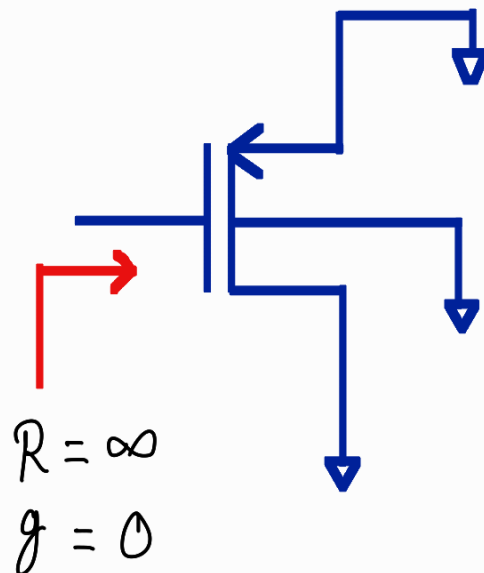

② Looking into Gate


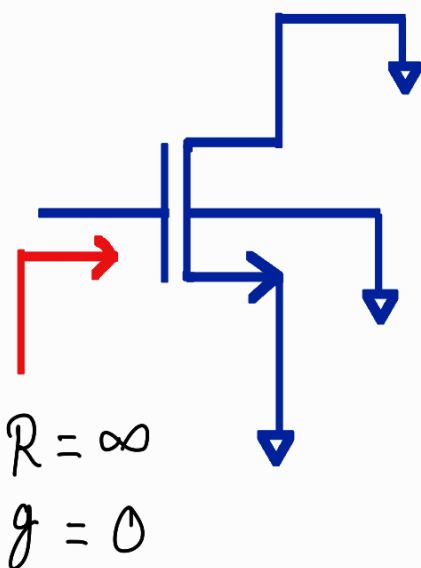


③

Looking into Source

$$R = \frac{1}{g_m} \parallel r_o \parallel \frac{1}{g_{mb}}$$

$$g = g_m + g_{mbs} + g_{ds}$$

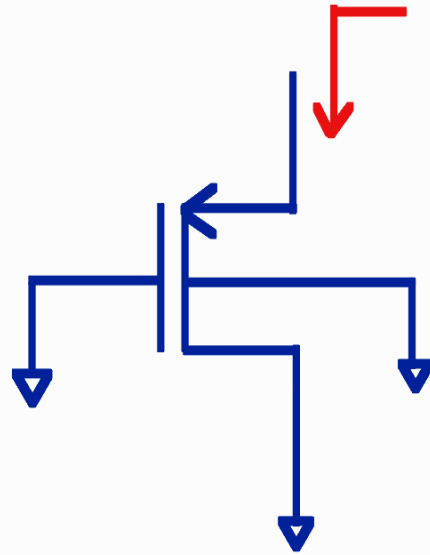
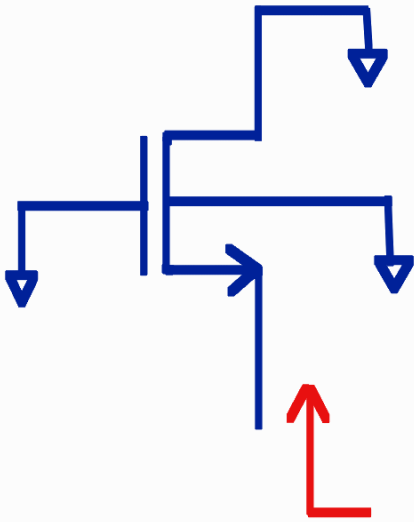


$$R = \frac{1}{g_m} \parallel r_o \parallel \frac{1}{g_{mb}}$$

$$g = g_m + g_{mbs} + g_{ds}$$

④

Looking into source (Self Biased Well)

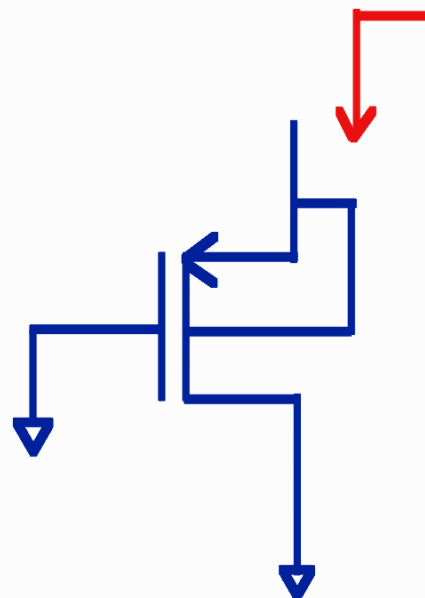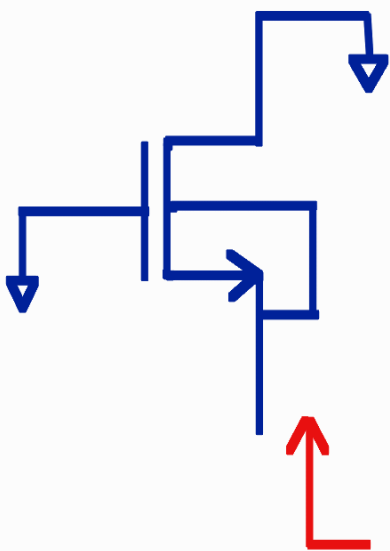

$$R = \frac{1}{g_m} \parallel r_o$$



$$g = g_m + g_{ds}$$

⑤

Diode connected

$$R = \frac{1}{g_m} \parallel r_o \approx \frac{1}{g_m}$$

$$g = g_m + g_{ds} \approx g_m$$

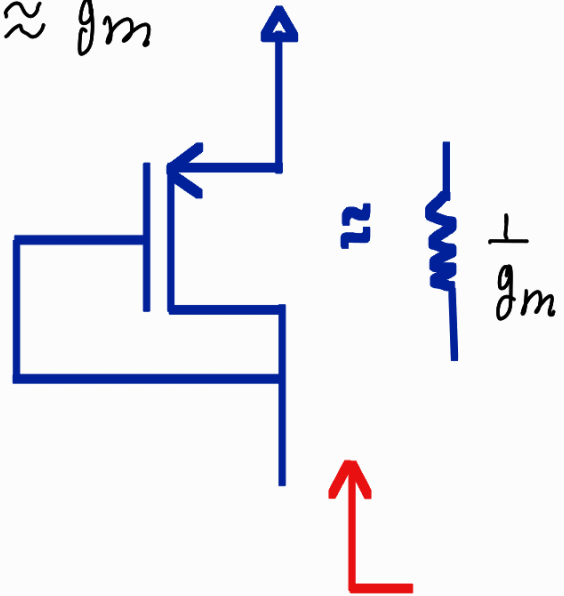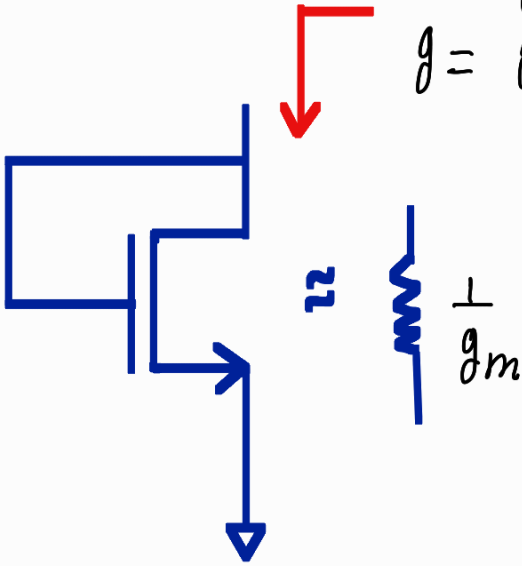


$$R = \frac{1}{g_m} \parallel r_o \approx \frac{1}{g_m}$$

$$g = g_m + g_{ds} \approx g_m$$

⑥

With RD

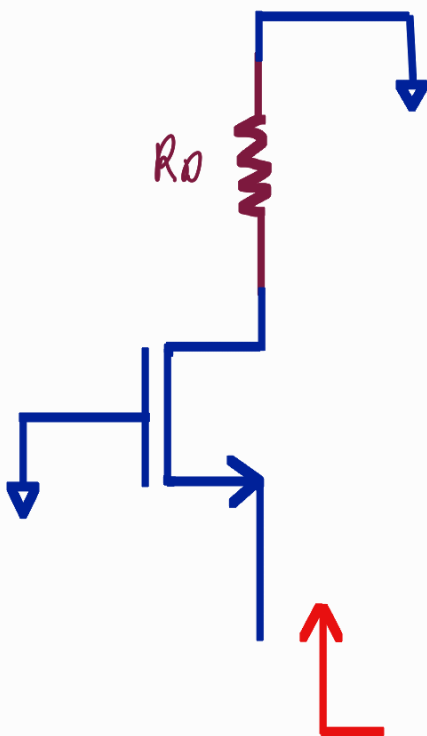

$$R = \frac{r_o + R_D}{1 + g_m r_o}$$


$$\approx \frac{1}{g_m} \quad R_D \ll r_o$$

if R_D is high then

$$R \neq \frac{1}{g_m}$$

7

Source Degeneration

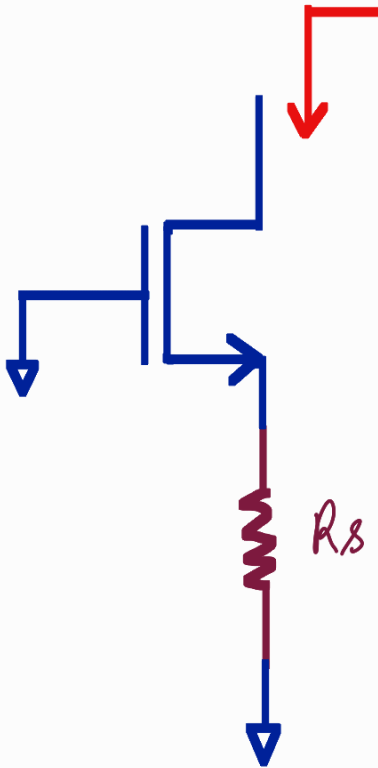


$$R = r_o + R_s (1 + g_m r_o)$$

$$\approx R_s (g_m r_o)$$

magnified by intrinsic gain

8

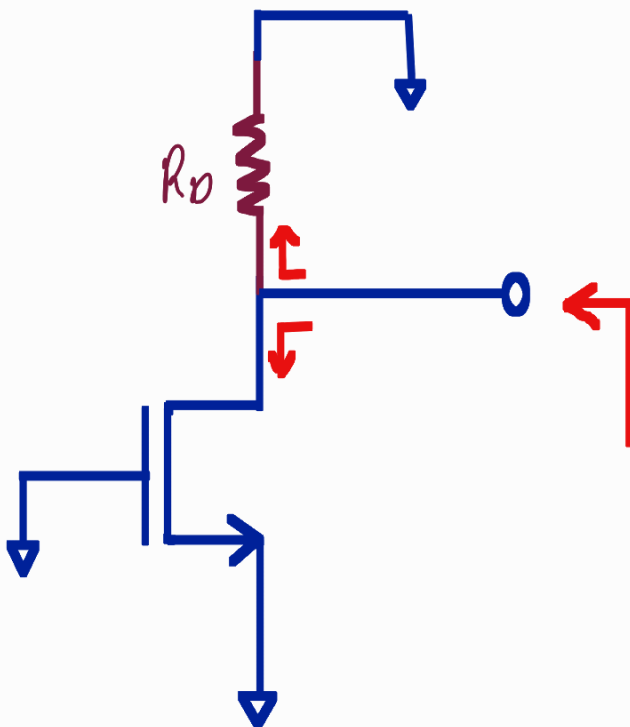


$$R = R_{up} \parallel R_{down}$$

$$= R_D \parallel r_o$$


$$\approx R_D$$

9

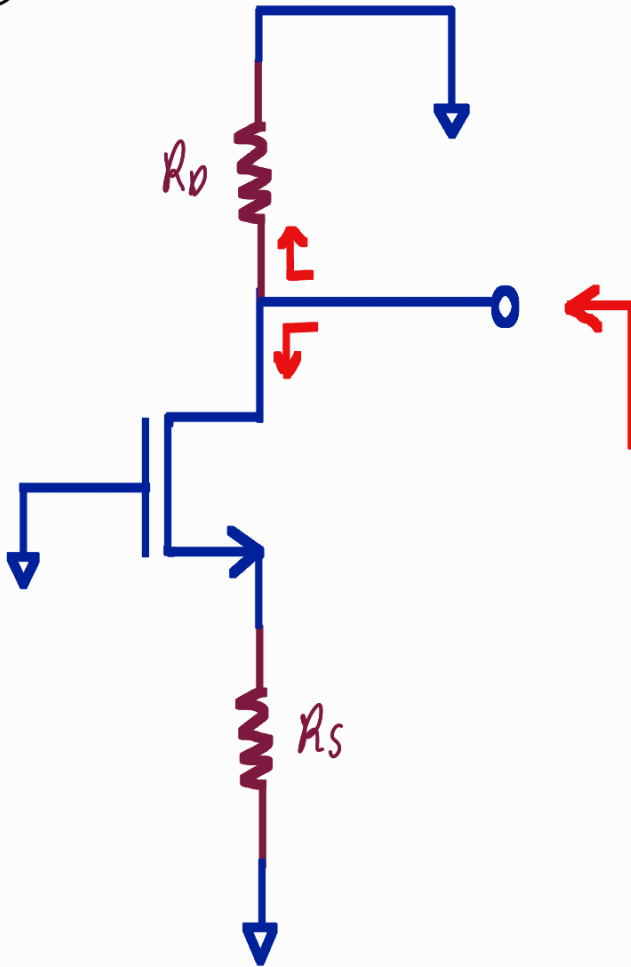


$$\begin{aligned}
 R &= R_{up} \parallel R_{down} \\
 &= R_D \parallel \underbrace{R_S (g_m r_o)}_{\text{high}} \\
 &\approx R_D
 \end{aligned}$$

10

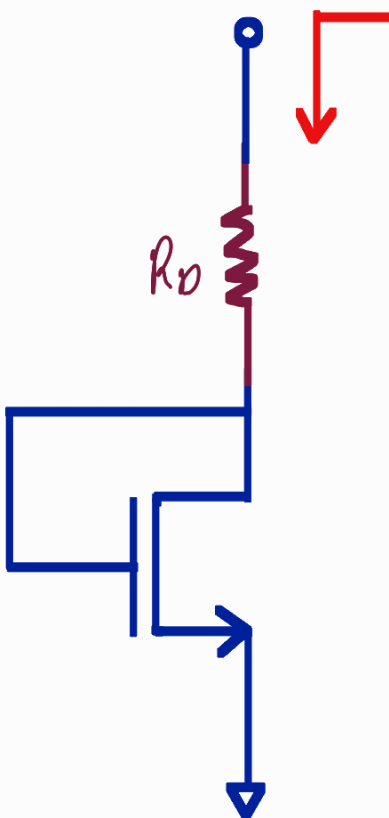

$$\begin{aligned}
 R &= R_D + \frac{1}{g_m} \parallel r_o \\
 R &\approx R_D + \frac{1}{g_m}
 \end{aligned}$$


11

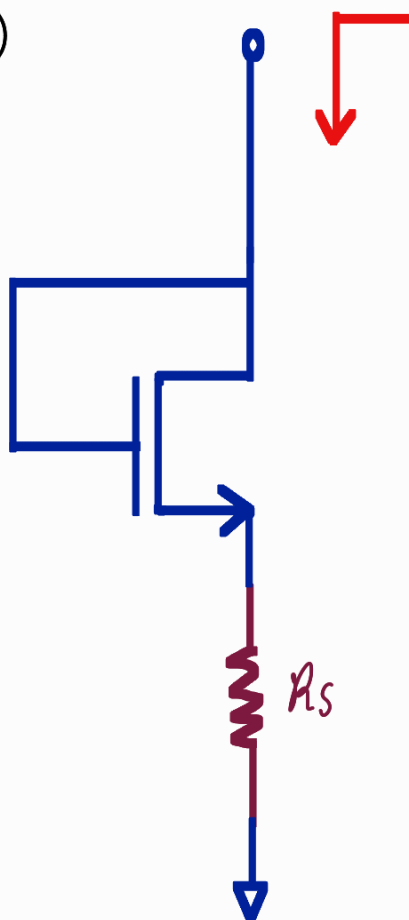

$$\lambda = 0$$

$$R = \frac{1}{g_m} + R_S$$


12

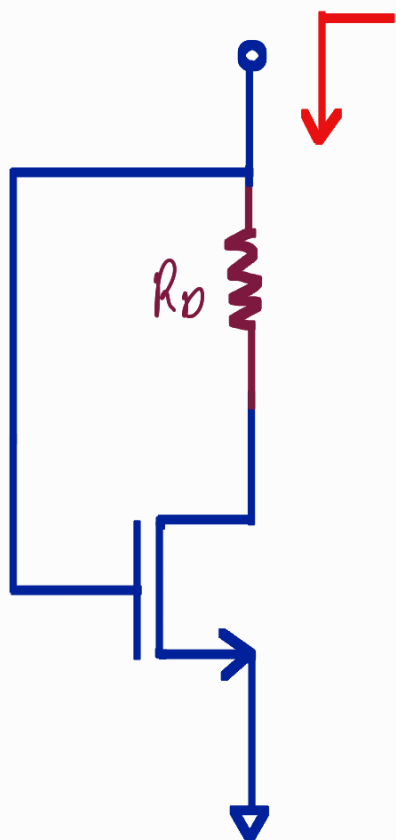

$$\lambda = 0$$

$$R = \frac{1}{g_m}$$

13

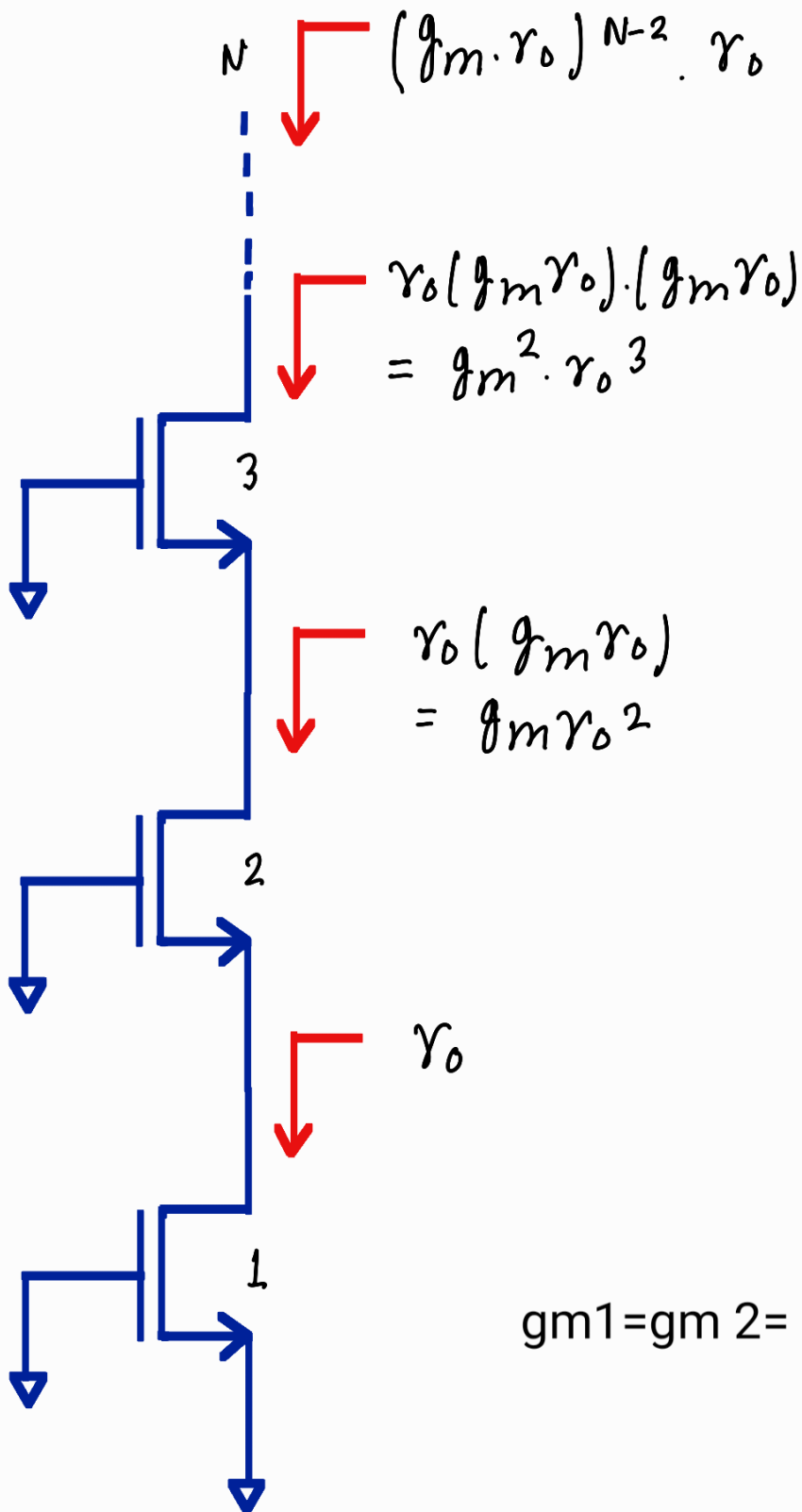

14

$$R = - \left(\frac{1}{g_{m1}} + \frac{1}{g_{m2}} \right)$$

$$= - \frac{2}{g_m} \quad \text{if } g_{m1} = g_{m2}$$

